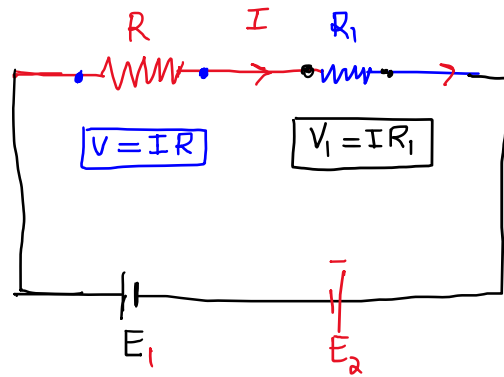


Applications of Linear System

Linear Equation and Network Circuits

Ohm Law:-




$$E = V + V_1$$

$$E_1 + E_2 = V + V_1$$

KIRCHHOFF'S VOLTAGE LAW

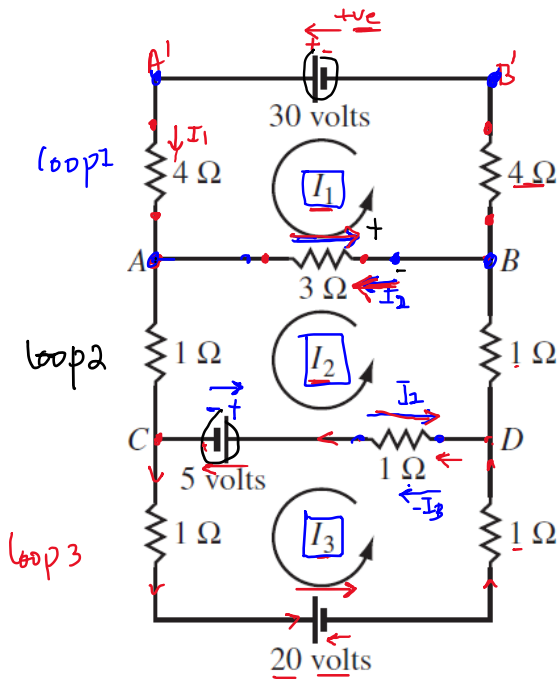The algebraic sum of the RI voltage drops in one direction around a loop equals the algebraic sum of the voltage sources in the same direction around the loop.



$$I_3 = -v_e$$

Example: Determine the loop currents in the electric circuit.

For loop 1:-

$$4I_1 + 3I_1 + 4I_1 - 3I_2 = 30$$

$$11I_1 - 3I_2 = 30$$

$$\begin{bmatrix} 11 & -3 & 0 & 30 \\ -3 & 6 & -1 & 5 \\ 0 & -1 & 3 & -25 \end{bmatrix}$$

For loop 2:-

$$-3I_1 + I_2 + I_2 + 3I_2 + I_2 - I_3 = 5$$


$$-3I_1 + 6I_2 - I_3 = 5$$

For loop 3

$$-I_2 + 3I_3 = -20 - 5 = -25$$

$$\begin{aligned} I_3 &= \\ I_2 &= \\ I_1 &= \end{aligned}$$

8.

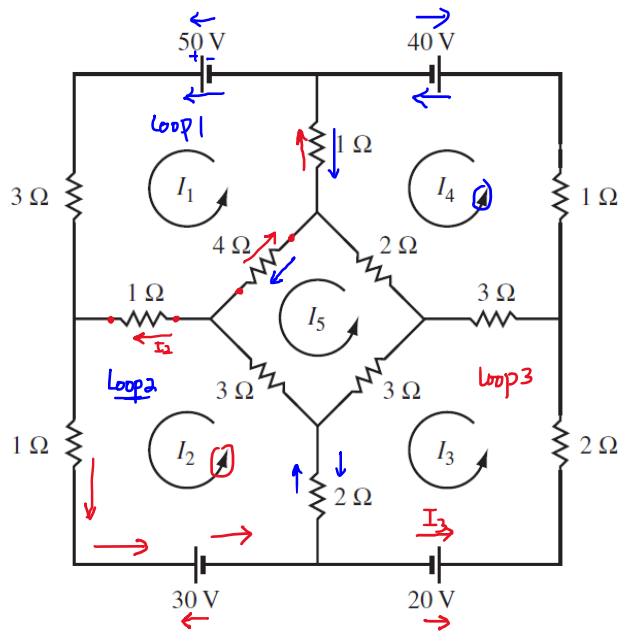

loop1:-

$$9I_1 - I_2 - 4I_5 - I_4 = 50$$

loop2:-

$$-I_1 + 7I_2 - 2I_3 - 3I_5 = -30$$

loop3

$$10I_3 - 2I_2 - 3I_5 - 3I_4 = 20$$

loop4

$$7I_4 - I_1 - 2I_5 - 3I_3 = -40$$

loop5

$$-2I_4 + 12I_5 - 4I_1 - 3I_2 - 3I_3 = 0$$

